

# CS232-Lab5

Hardik Rajpal - 200050048

February 2022

## 1 10-Modulo Counter

I used three important signals `nextCount`, `incrNextCount` and `decrNextCount` to store different cases of the inputs. First, I used 4-bit full adder-subtractors to obtain `incrNextCount` and `decrNextCount` from `nextCount`. Then, I used nested if blocks in a process with sensitivity variables `clk` and `rst`. I had to explicitly account for edge cases (when the count was close to 0 or 9) but otherwise I used the outputs from the 4-bit full adder-subtractors.

Finally there is a single process sensitive to `rst` and `nextCount` that updates the output pin of count with `nextCount` when it's changed.